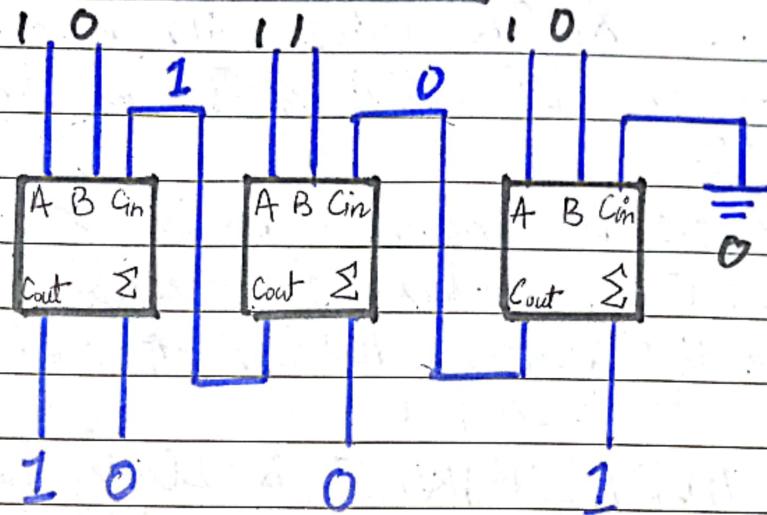


Assignment # 5

Question # 01

a)




Long Hand Addition:

$$\begin{array}{r}
 A : 1 \ 1 \ 1 \\
 B : 0 \ 1 \ 0 \\
 \hline
 \text{Sum} : 1 \ 0 \ 0 \ 1
 \end{array}$$

b)

~~Question number~~

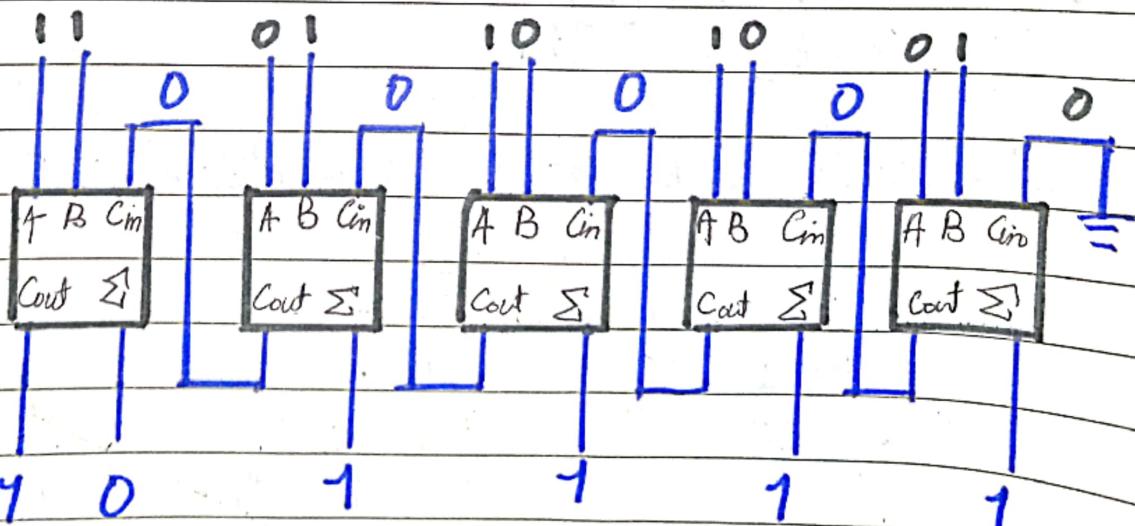

$$\begin{array}{r}
 A : 1 \ 0 \ 1 \ 1 \ 0 \\
 B : 1 \ 1 \ 0 \ 0 \ 1 \\
 \hline
 \text{Sum} : 1 \ 0 \ 1 \ 1 \ 1
 \end{array}$$

Pg No.

$$\begin{array}{r}
 \text{Sum} : 1 \ 0 \ 1 \ 1 \ 1
 \end{array}$$

Sandal

Question # 2

Q) When the ADD/SUBTRACT input is HIGH, the bits of number B gets inverted due to the attached XNOR gates with them. Moreover, the C_{in} of the 1st adder gets an input of 1 rather than 0.

Therefore, the number B is changed into its 2's complement and added with number A, which will yield the difference between A and B. The last carry is also discarded.

b) When ADD/SUBTRACT is LOW, the circuit will behave like a normal adder without changing the bits of B and the input carry. Last carry is also discarded.

c) Assuming: ADD/SUBTRACT = 1, | | | |
 A = 1010 | | | |
and B = 1101 | | | |

2's
↓
| | | | | | | | | | | | | |

* The circuit will change B into its complement because ADD/SUBTRACT is high:

$$\Rightarrow B_{2^1} = 0011$$

* The circuit will now add B_{2^1}'s and A:

$$A : \begin{array}{r} 1 \\ 0 \\ 1 \\ 0 \end{array}$$

$$B : \begin{array}{r} 0 \\ 0 \\ 1 \\ 1 \end{array}$$

$$\text{Sum} : \begin{array}{r} 1 \\ 1 \\ 0 \\ 1 \end{array}$$

is the output

Question # 3

A₁

A₂

B₁

B₂

Cin

Sum 1

Sum 2

~~Cout~~

Cout

t₀ t₁ t₂ t₃ t₄ t₅ t₆ t₇ t₈

Question # 4

Cin : 0 0 0 0
↓ ↓ ↓ ↓

A₁ 1 0 1 0

B₁ 1 0 0 1

Σ_1 0 0 1 1

1 1 0 0 1 0 } carries
↓ ↓ ↓ ↓

A₂ 1 1 0 0

B₂ 1 0 1 1

Σ_2 1 1 1 1

A₃

B₃

Σ_3

A₄

B₄

Σ_4

1 0 0 0 carries
↓ ↓ ↓ ↓

0 1 0 1

0 0 0 0

1 1 0 1

0 1 1 0 } carries
↓ ↓ ↓ ↓

1 1 0 1

0 0 0 1

1 1 0 0

↓ ↓ ↓ ↓


Cout: 0 0 0 1

Hence:

$$\begin{array}{l} \Sigma_0: 0011 \\ \Sigma_1: 1111 \\ \Sigma_2: 1101 \\ \Sigma_3: 1100 \\ \text{Cout: } 0001 \end{array}$$

Question # 5

A0

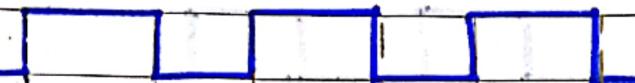


A1




B0



B1

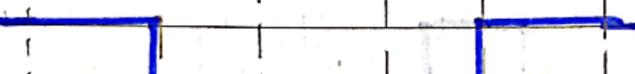


A = B

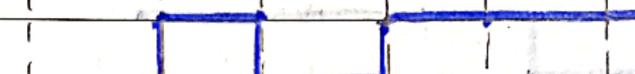

Question # 6

a)

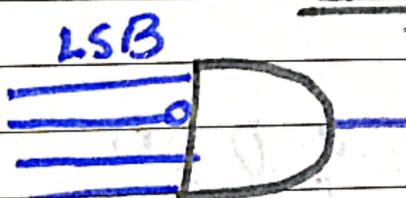


For 1101

b)




For 1000

c)

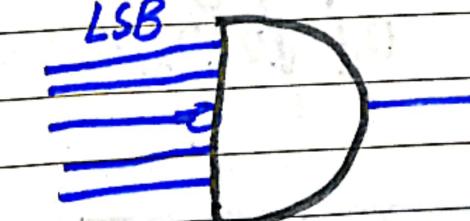

For 11011

d)

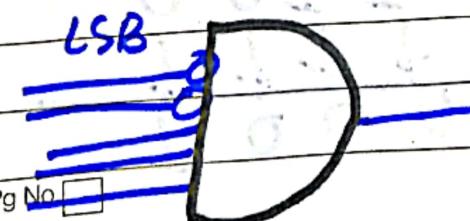

For 11100




Question # 6

A0				
A1				
A2				
A3				
B0				
B1				
B2				
B3				
$A > B$				
$A = B$				
$A < B$				

a) LSB




Question # 8

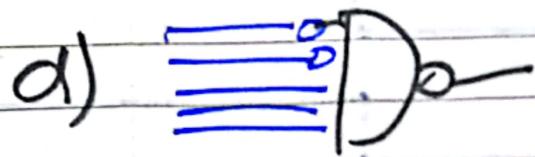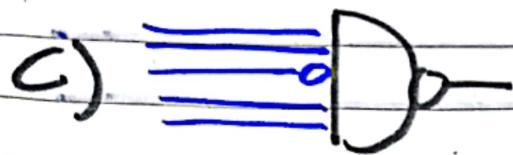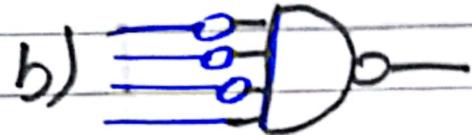

Question # 9


Equation: $A\bar{B}C + AB\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D$

Circuit:

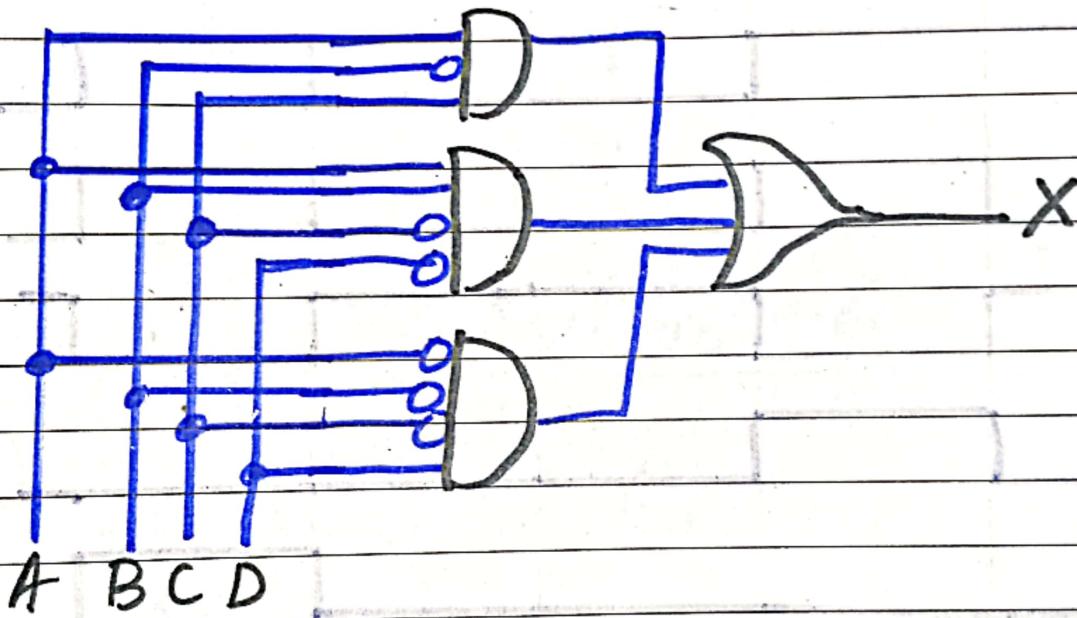


Question # 10

A_0

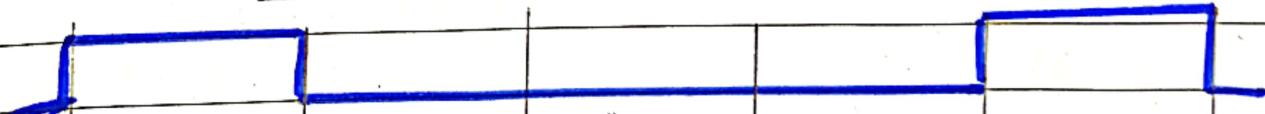

A_1

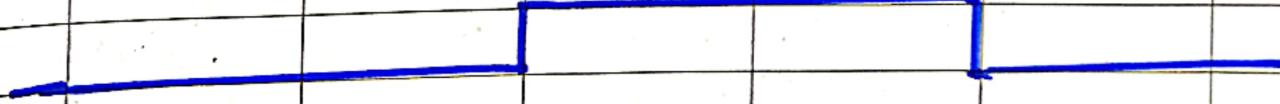

t_3



Y



Pg No.

Pg No.

Question # 11

A₀

A₁

A₂

A₃

0

1

2

3

4


5

6


7

8

9

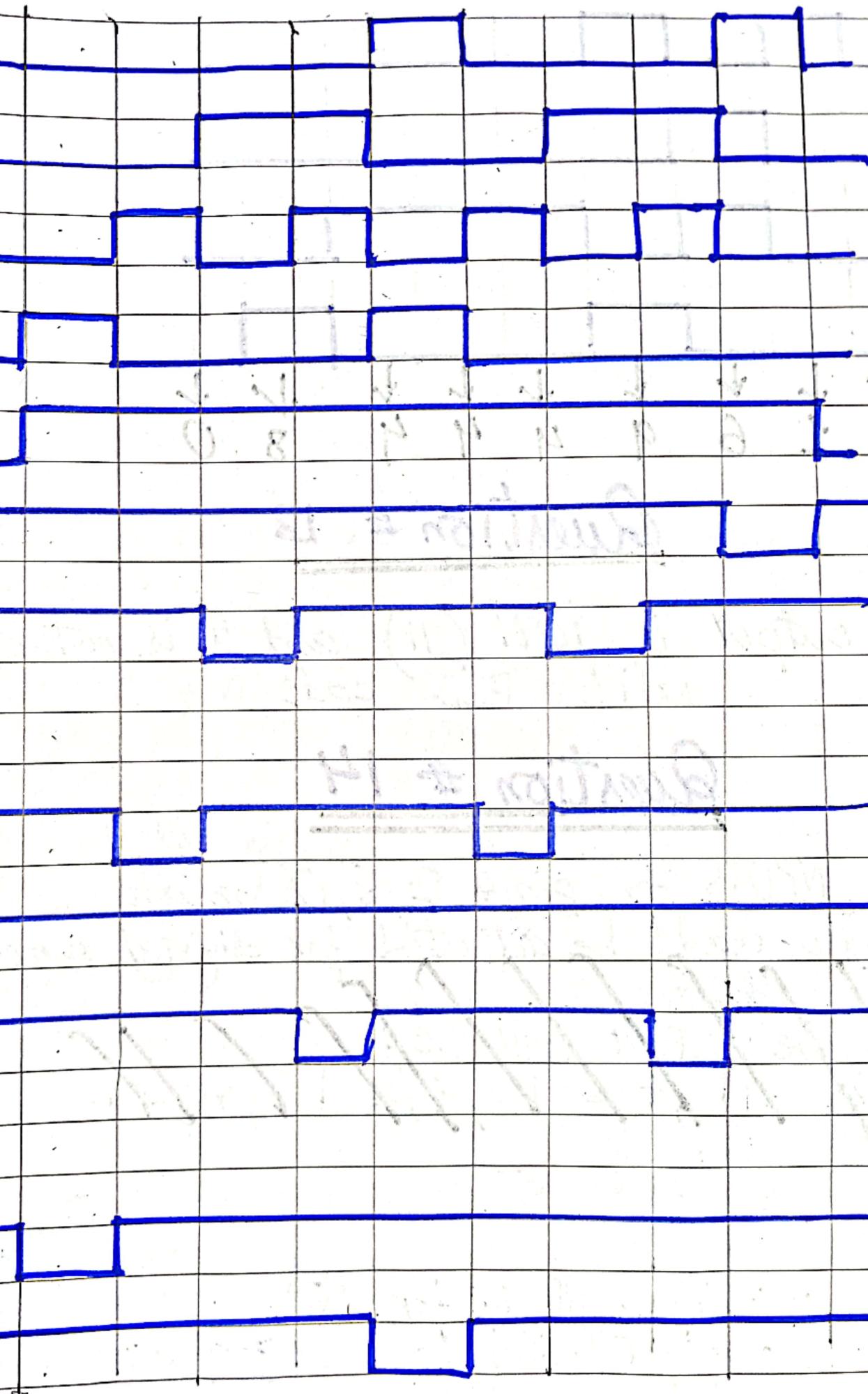

Question #12

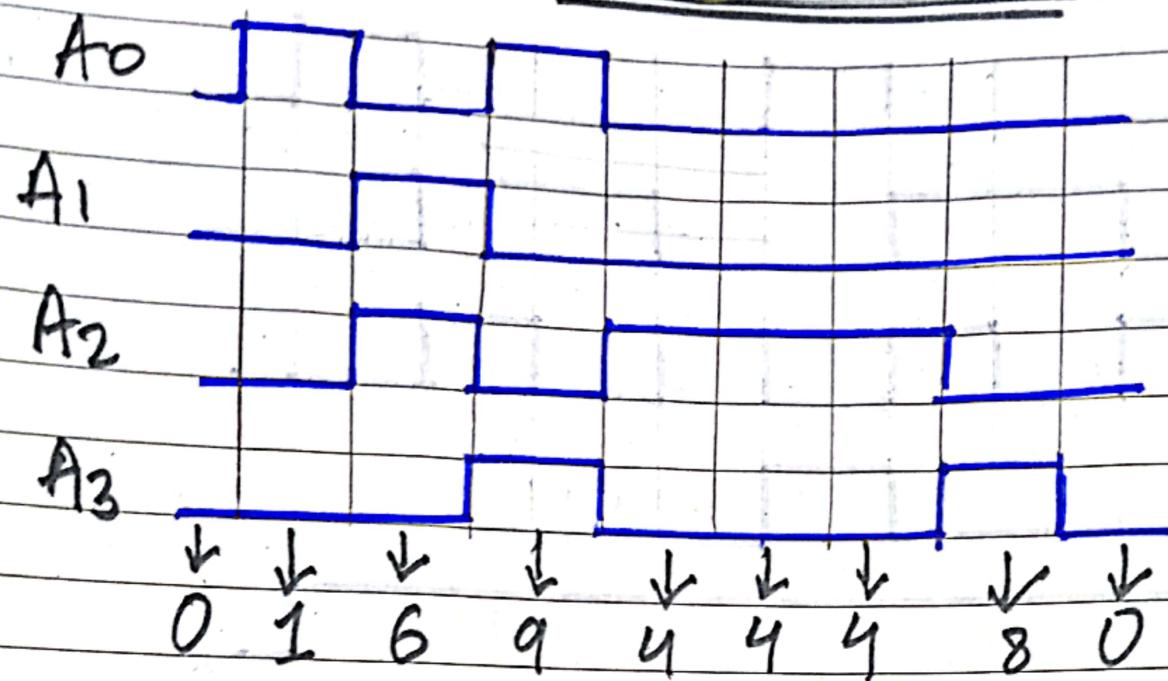

Question # 13

The output is 1011 (11) and it is not a valid BCD code

Question # 14

* LOW INPUTS on pins # 2, 5, 12 means the logic should be activated for digital numbers:

2, 5, and 8.
Hence, the output will be:
 $A_0 = 1, A_1 = 1, A_2 = 1, A_3 = 1$

2 and 5

⇒ The priority will be for '5'
i.e. the output will be as ~~A₀A₁A₂A₃~~ 0101


Question # 16

Truth Table:

A	B	C	X
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

SOP: $\bar{A}\bar{B}C + \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}\bar{C}$


K-Map:

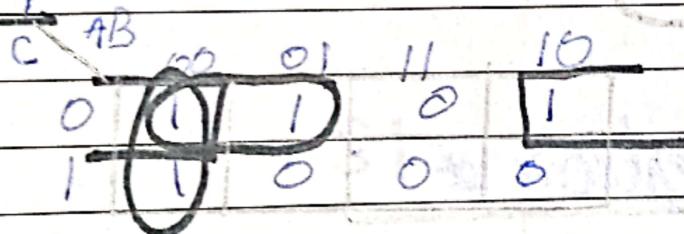

$$\Rightarrow \bar{A}\bar{B} + \bar{A}C + \bar{B}\bar{C}$$

$$\Rightarrow (\bar{A}+B) + (\bar{A}+C) + (B+C)$$

Circuit:

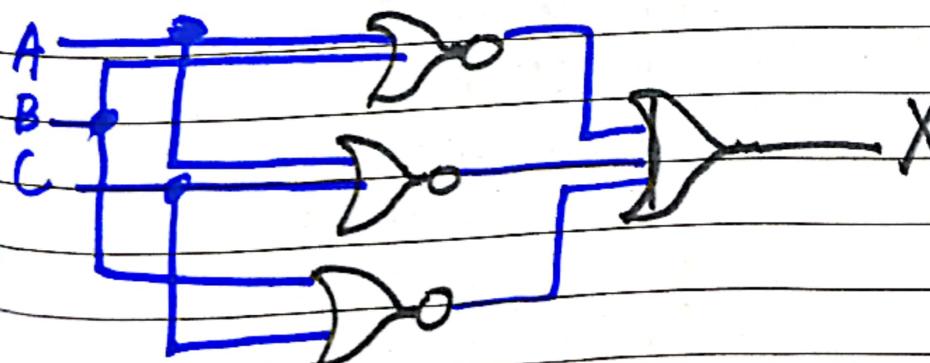


Question # 16


* K-Map:

C\AB	00	01	11	10
0	1	0	0	0
1	0	0	1	0

$$\Rightarrow \overline{ABC} + ABCD$$

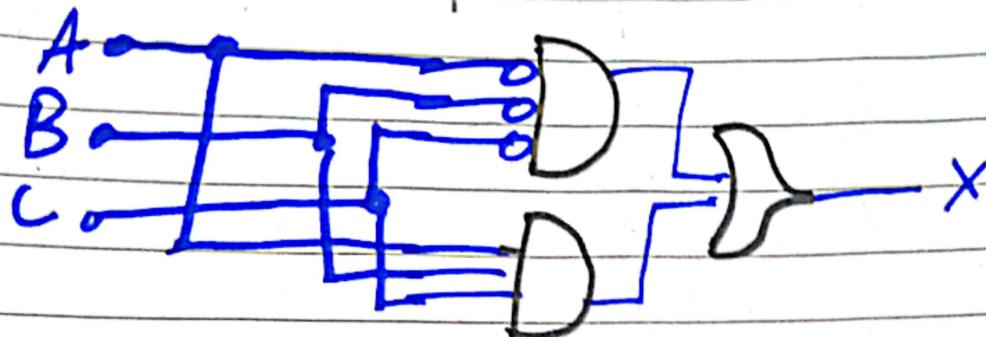

Question # 17

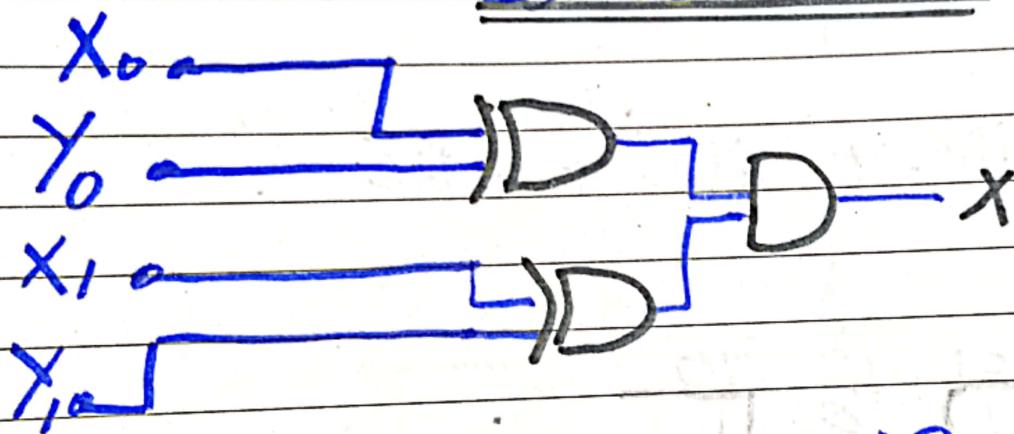

Question # 18

$A_3\ A_2\ A_1\ A_0\ X$

0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
1	1	1	1	1

$A_3\ A_2\ A_1\ A_0\ X$

1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0


K-Map:

Date: _____

		A ₃ A ₂	A ₃ A ₂	A ₃ A ₂	
		00	01	11	10
00		0	0	1	0
01		1	1	1	1
11		0	0	0	0
10		0	0	0	0

$$\Rightarrow \bar{A}_3 A_2 + \bar{A}_3 A_1 A_0$$

Circuit:

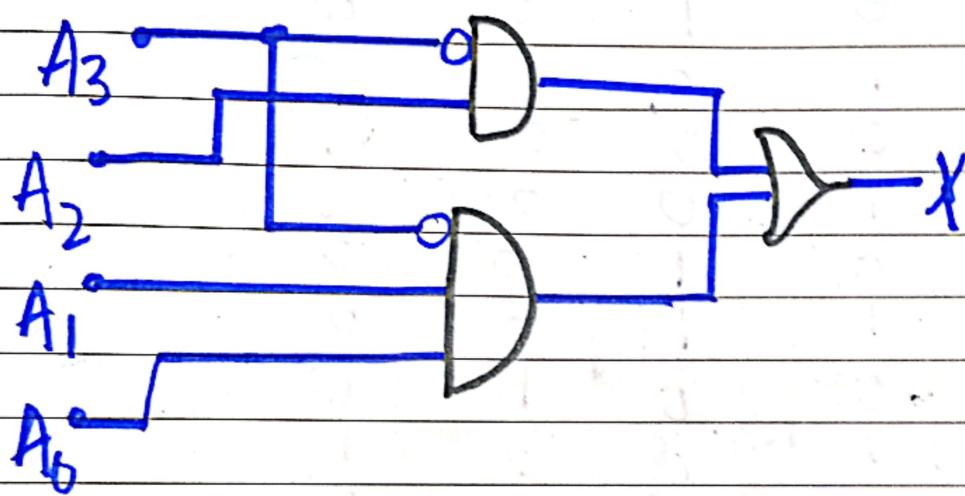

Question # 19



Diff

+ B ~~Sum~~ Early Functions

0	0	0	0	AB
0	1	1	1	$\bar{A}B$
1	0	1	0	$\bar{A}\bar{B}$
1	1	0	0	AB

$$\text{Diff.} = \bar{A}B + A\bar{B} = A \oplus B$$

$$\text{Carry} = \bar{A}B$$

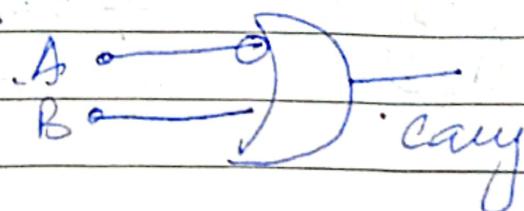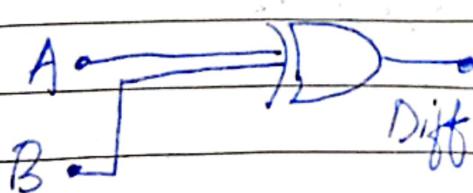

Question # 20

A_2	A_1	B_2	B_1	$A > B$	$A = B$	$A < B$
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	0	1
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	0	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

~~$A \bar{A}_2 \bar{B}_1 \bar{B}_2 + \bar{A}_2 \bar{B}_1 B_2 + A_2 \bar{B}_1 B_2 + A_2 B_1 \bar{B}_2 + A_2 B_1 B_2$~~

~~$+ A_2 \bar{A}_1 B_2 \bar{B}_1 + A_2 \bar{A}_1 B_2 B_1 + A_2 A_1 \bar{B}_2 \bar{B}_1 + A_2 A_1 \bar{B}_2 B_1$~~

$A > B$:

$A_2 A_1$	$\cancel{B_2 B_1}$					
	00	00	00			
	01	01	00			
	11	11	01			
	10	10	00			

$\Rightarrow A_2 A_1 \bar{B}_1 + \bar{B}_2 \bar{B}_1 \cdot A_1 + A_2 \bar{B}_2$

A = B:

A_2A_1	B_2B_1	00	01	11	10
00	1	0	0	0	0
01	0	1	0	0	0
11	0	0	1	0	0
10	0	0	0	1	0

$$\Rightarrow \overline{A_2}\overline{A_1}B_2\overline{B_1} + \overline{A_2}\overline{A_1}\cdot\overline{B_2}B_1 \\ + A_2\overline{A_1}B_2B_1 + A_2\overline{A_1}\cdot\overline{B_2}B_1$$

$$\Rightarrow (\overline{A_1} \oplus \overline{B_1})(\overline{A_2} \oplus \overline{B_2})$$

A < B:

A_2A_1	B_2B_1	00	01	11	10
00	0	1	(1)	(1)	1
01	0	0	(1)	(1)	1
11	0	0	0	0	0
10	0	0	A	0	0

$$\Rightarrow \overline{A_2}\overline{A_1}B_1 + \overline{A_1}B_1B_2 + \overline{A_2}B_2$$

Question # 21

A	B	C	D	a	b	c	d	e	f	g	j
0	0	0	0	1	1	1	1	1	1	1	0
0	0	0	1	0	1	1	0	0	0	0	0
0	0	1	0	1	1	0	1	1	0	1	
0	0	1	1	1	1	1	1	0	0	1	
0	1	0	0	0	1	1	0	0	1	1	
0	1	0	1	1	0	1	1	0	1	1	
0	1	1	0	1	0	1	1	1	1	1	
0	1	1	1	1	1	0	0	0	0	0	
1	0	0	0	1	1	1	1	1	1	1	
1	0	0	1	1	1	1	1	0	1	1	
1	0	1	0	0	0	0	0	0	0	0	0
1	0	1	1	0	0	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0	0	0	0
1	1	0	1	0	0	0	0	0	0	0	0
1	1	1	0	0	0	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0	0
Pg. No.				0	0	0	0	0	0	0	0
				1	0	0	0	0	0	0	0

AB		CD	
00	00	00	11
01	01	01	10
11	11	00	01
10	10	11	00

a:

AB		CD	
00	00	00	11
01	01	01	10
11	11	00	00
10	10	11	00

$$\Rightarrow a = \bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C} + \\ \bar{A}BD + \bar{A}C$$

b:

AB		CD	
00	00	01	11
01	01	01	00
11	11	00	00
10	10	11	00

$$\Rightarrow \bar{A}\bar{B} + \bar{A}\bar{C}\bar{D} + \bar{A}\bar{C}D + \bar{B}\bar{C}$$

c:

AB		CD	
00	00	01	11
01	01	11	10
11	11	00	00
10	10	11	00

d:

AB		CD	
00	00	01	11
01	01	01	00
11	11	00	00
10	10	11	00

e:

AB		CD	
00	00	00	11
01	01	00	10
11	11	00	00
10	10	00	00

$$\Rightarrow \bar{B}\bar{C}\bar{D} + \bar{A}\bar{C}\bar{D}$$

	00	01	11	10
01	0	0	0	0
11	0	0	0	0
10	0	1	0	0

$$\Rightarrow \bar{B}CD + \bar{C}AB + \bar{A}BC + \bar{B}BD$$

	00	01	11	10
01	0	0	0	1
11	0	0	0	0
10	1	0	0	0

$$\Rightarrow \bar{A}\bar{B}C + A\bar{B}\bar{C} + ABC + ACD$$

$$\text{Hence } a = A\bar{B}\bar{C} + \bar{A}BD + \bar{A}C + BCD$$

$$b = \bar{A}\bar{B} + \bar{A}\bar{C}\bar{D} + \bar{A}CD + \bar{B}\bar{C}$$

$$c = \bar{B}\bar{A}\bar{C} + \bar{A}\bar{D} + \bar{A}B + \bar{B}\bar{C}$$

$$d = A\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{D} + \bar{A}CD + \bar{B}\bar{C}\bar{D}$$


$$e = \bar{A}CD + \bar{B}\bar{C}\bar{D}$$

$$f = A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}BD + \bar{B}\bar{C}\bar{D}$$


$$g = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{B}\bar{C}\bar{D}$$

Circuit Diagrams:


a:

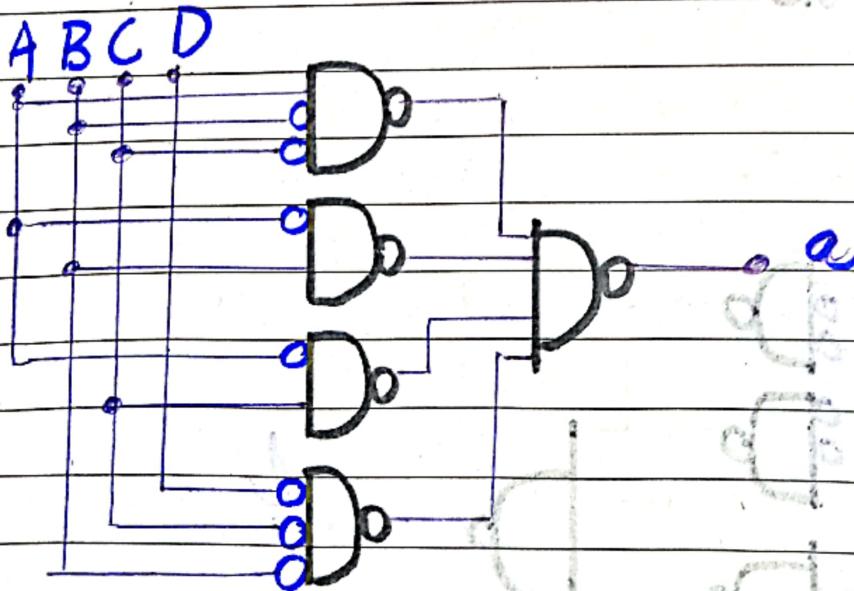


b:

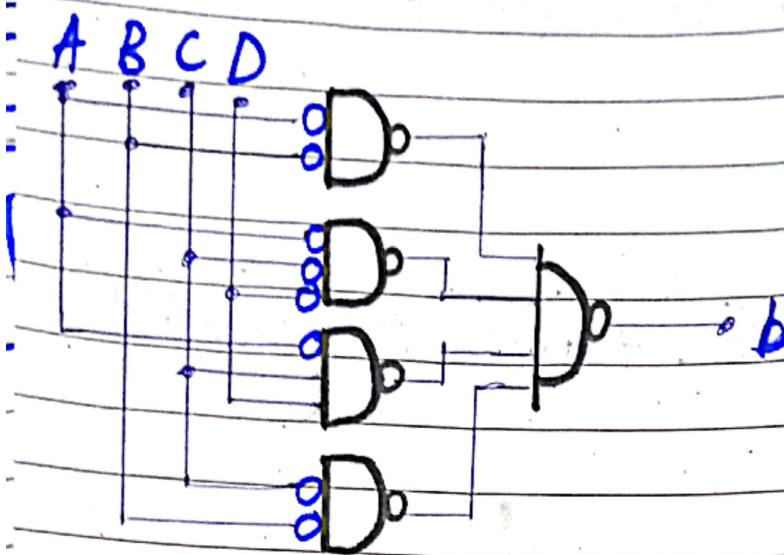



c:

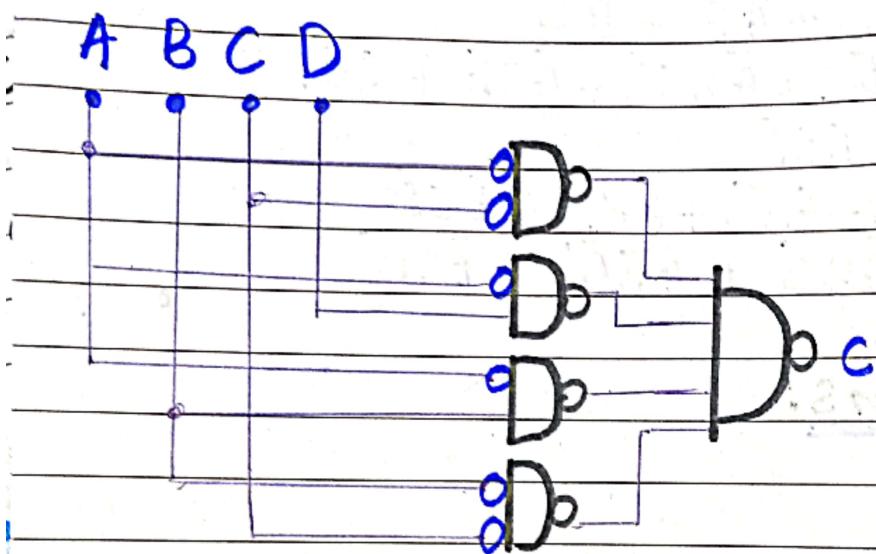

d:


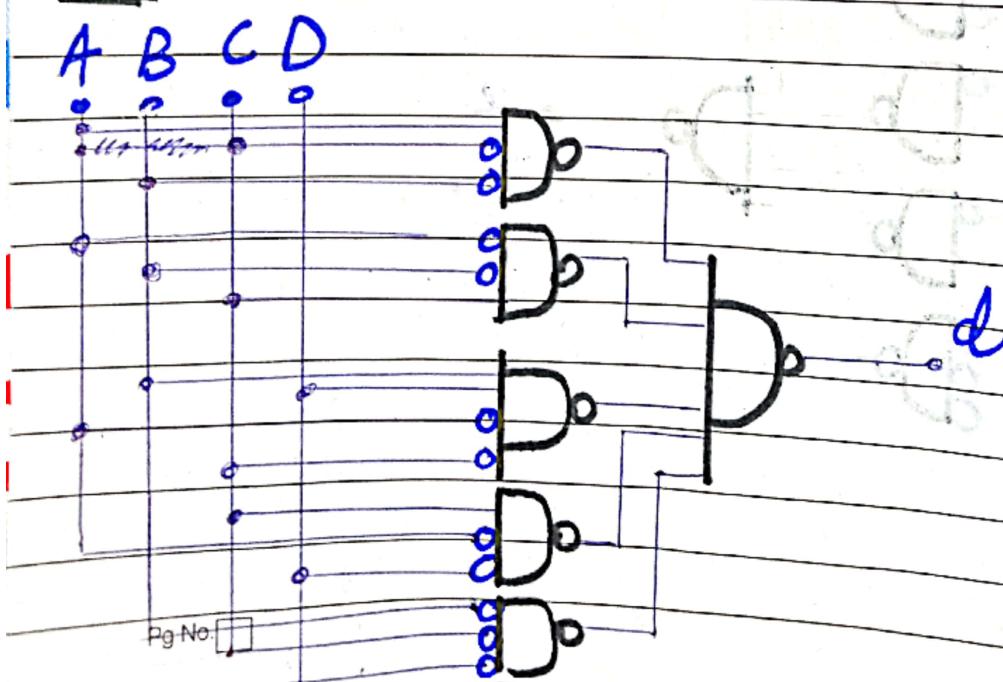


e:

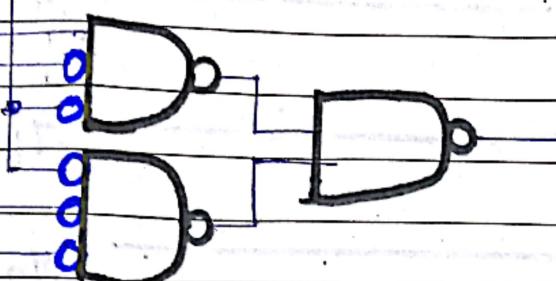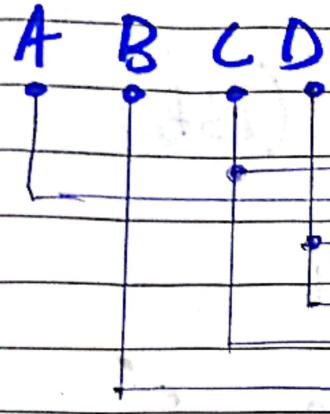



f:

A B C D

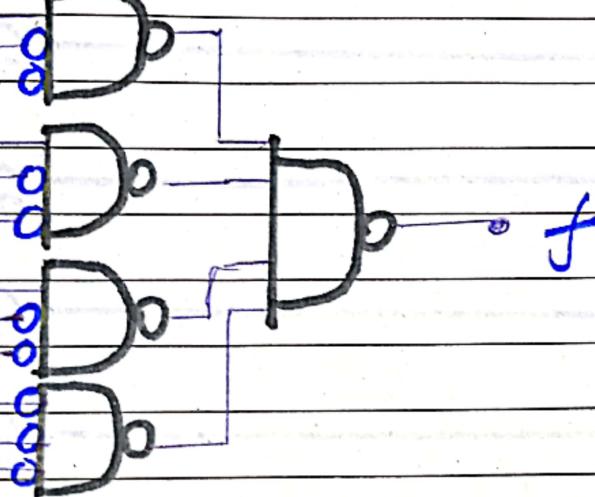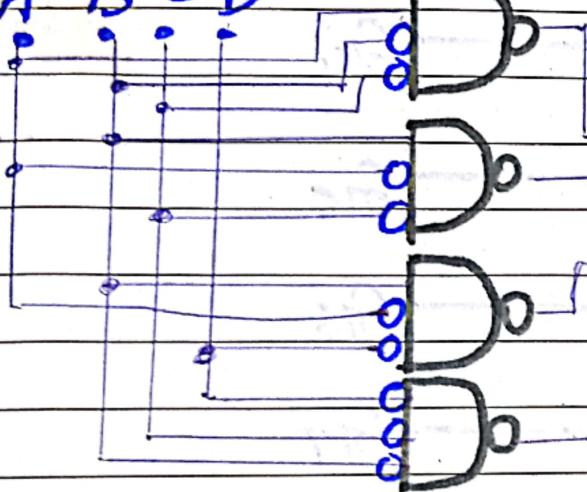


g:

A B C D

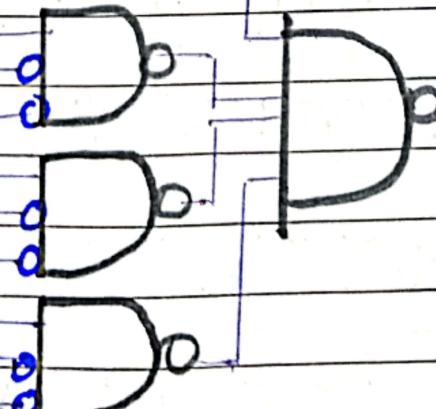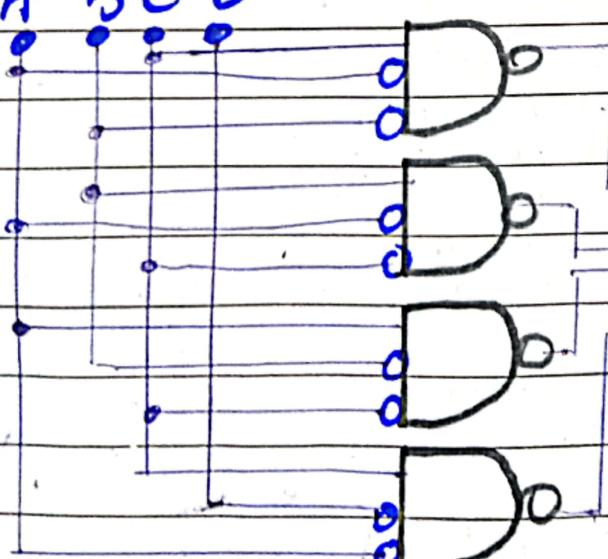

Question # 22

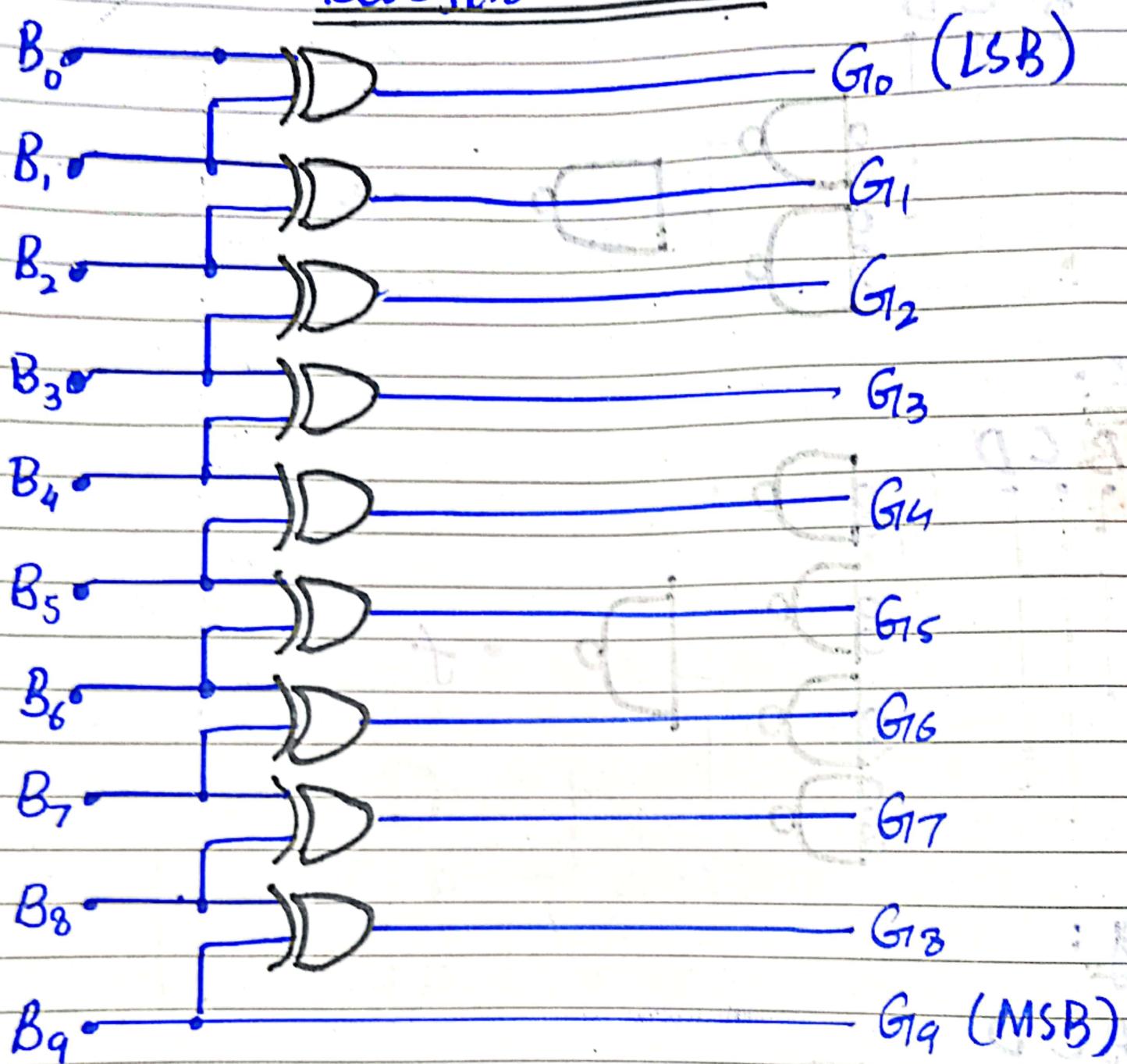


a) $101011100 \rightarrow 111100010$

b) $111000011 \rightarrow 1000100010$

c) $101110011 \rightarrow 1110001010$

d) $100000001 \rightarrow 100000001$

Question # 23

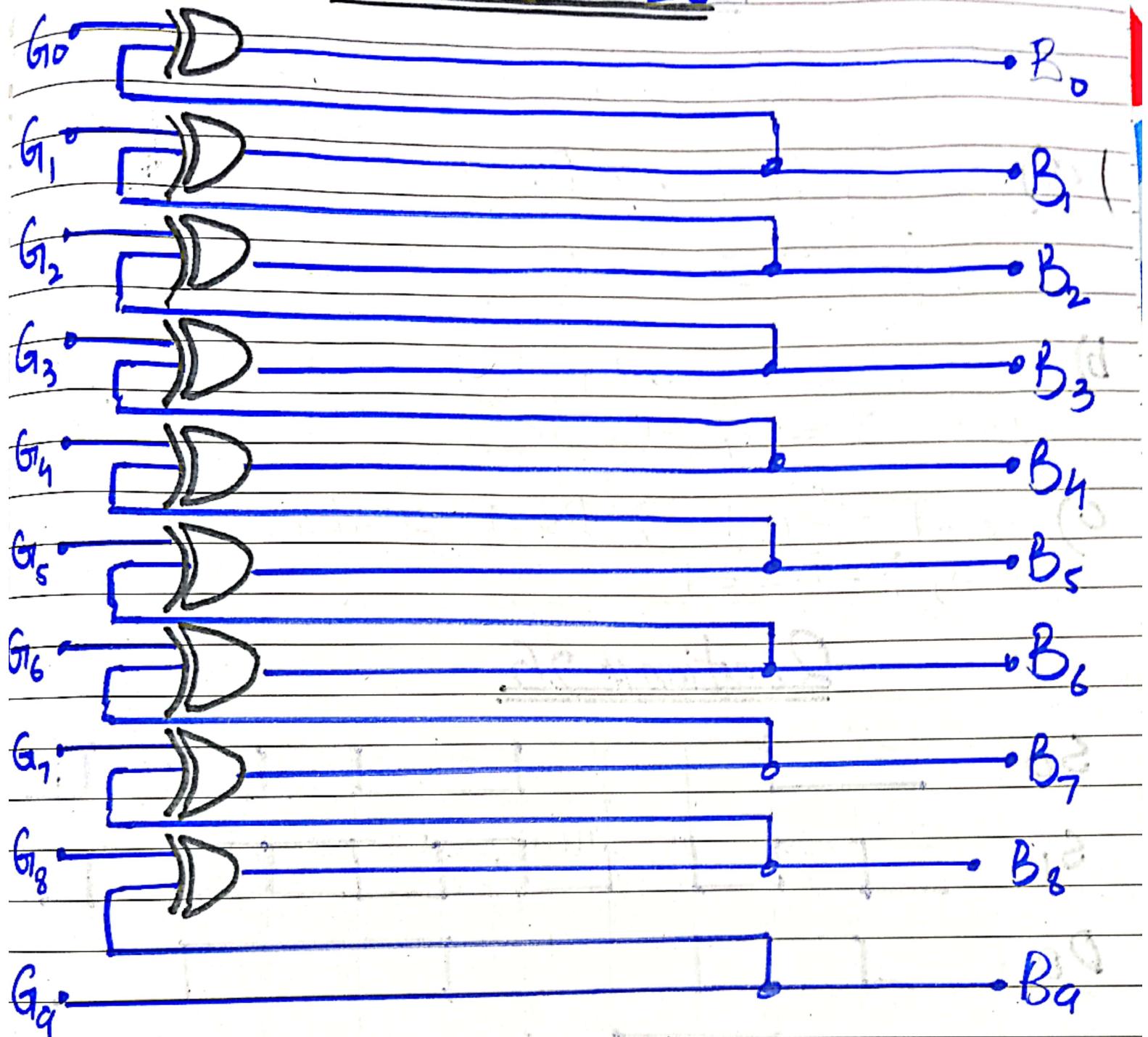

a) $1010111100 \rightarrow 1100101000$

b) $1111000011 \rightarrow 1010000010$

c) $101110011 \rightarrow 1101010000$

d) $100000001 \rightarrow 111111110$

Question # 24

$$D_0 = 1, D_1 = 0, D_2 = 0, D_3 = 1$$

a) $S_0 = 0, S_1 = 1 \Rightarrow D_2$ is enabled

Therefore, $Y = D_2 = 0$

b) $S_0 = 1, S_1 = 0 \Rightarrow D_1$ is enabled

Thus, $Y = D_1 = 0$

c) $S_0 = 1, S_1 = 1 \Rightarrow D_3$ is enabled

Thus, $Y = D_3 = 1$

Question # 25

S_0

S_1


D_0

D_1


D_2

D_3

Y

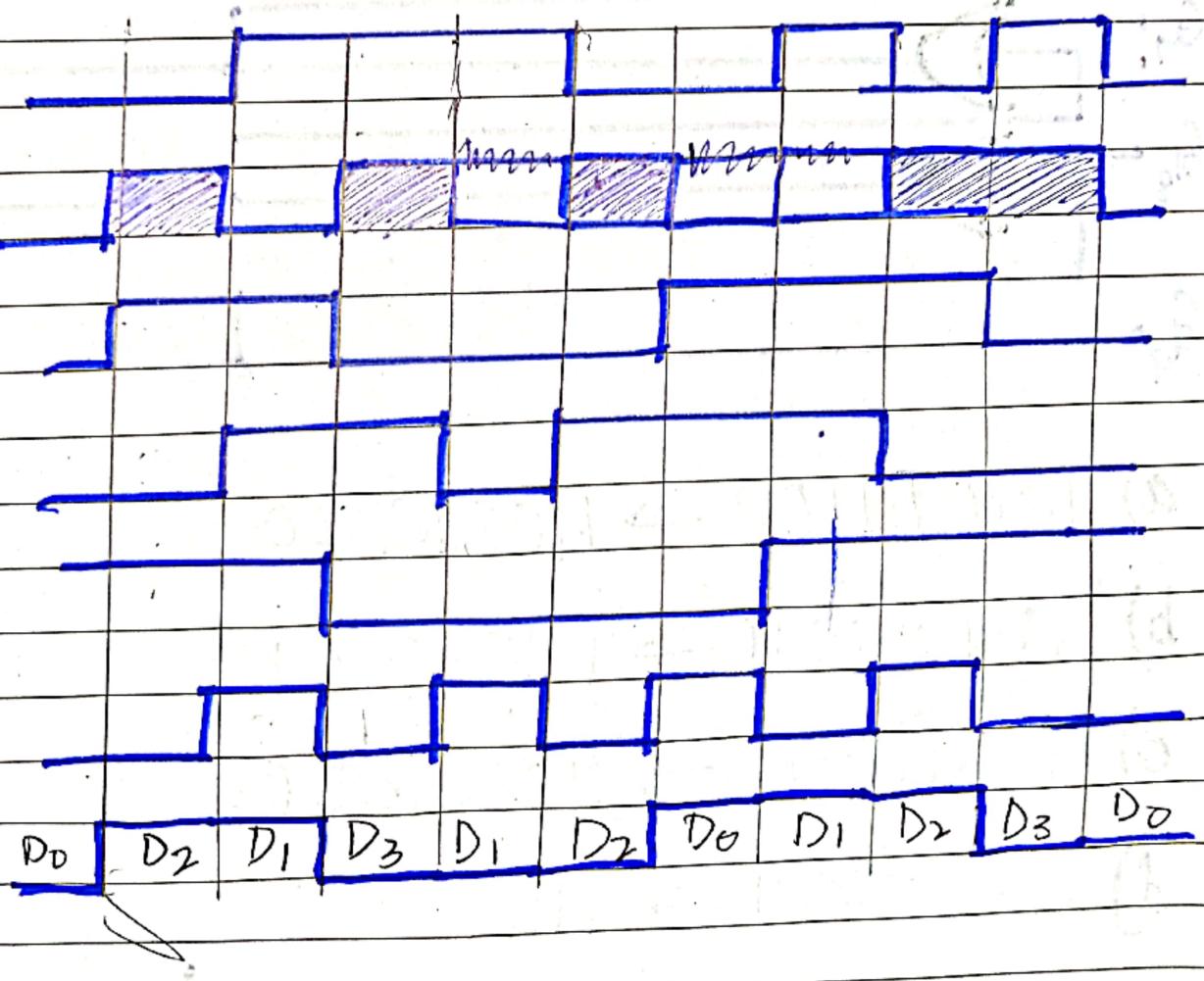


Question # 26

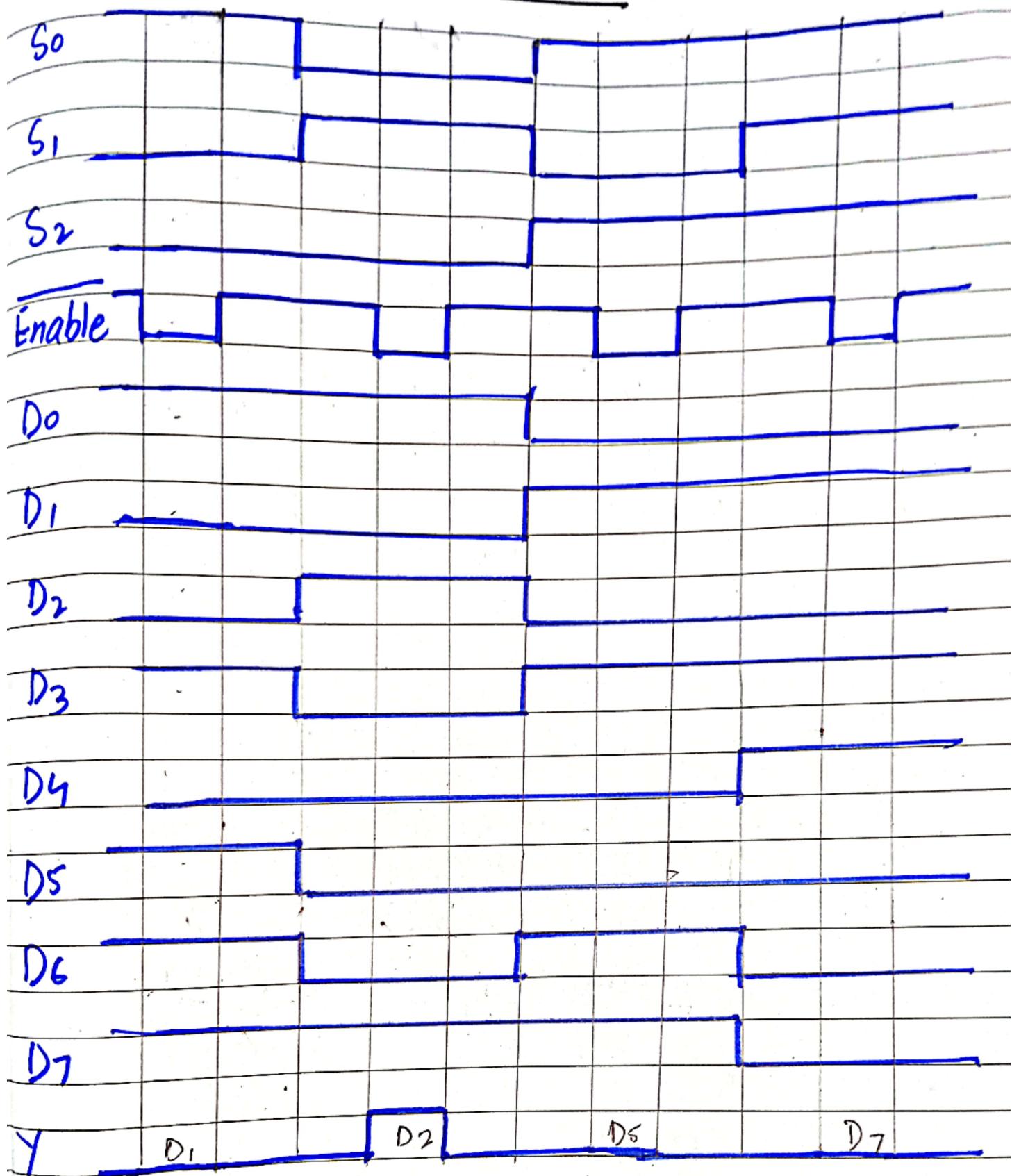

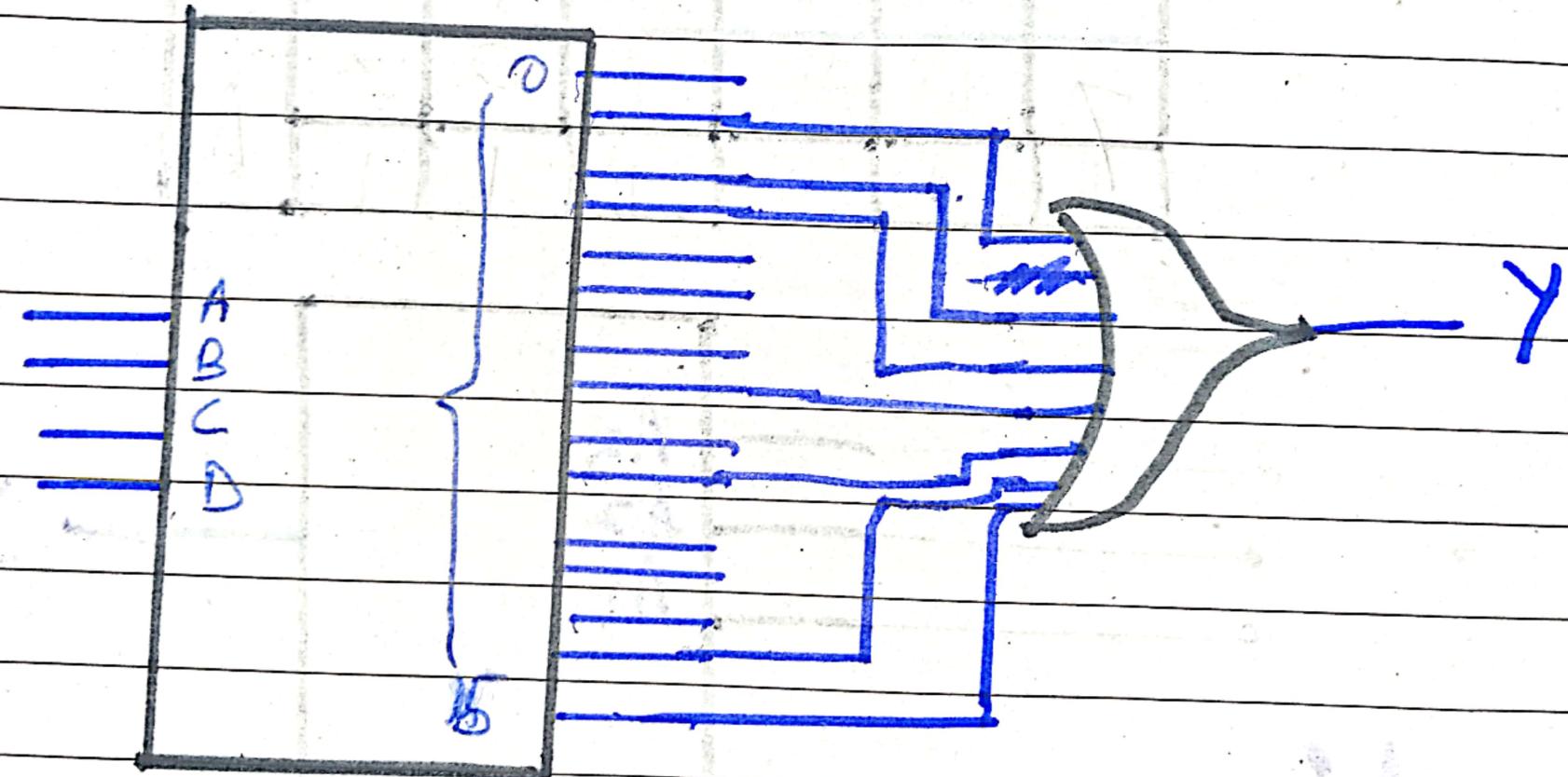
Question # 28

$$F(A, B, C, D) = \sum(1, 2, 3, 7, 9, 13, 15)$$



Question # 29


	A_3	A_2	A_1	A_0	Y
0	0	0	0	0	0
0	0	0	1	0	0
1	0	0	1	0	1
1	0	0	1	1	1
2	0	1	0	0	1
2	0	1	0	1	0
3	0	1	1	0	0
3	0	1	1	1	0
4	1	0	0	0	1
4	1	0	0	1	1
5	1	0	1	0	1
5	1	0	1	1	1
6	1	1	0	0	0
6	1	1	0	1	0
7	1	1	1	0	0
7	1	1	1	1	1

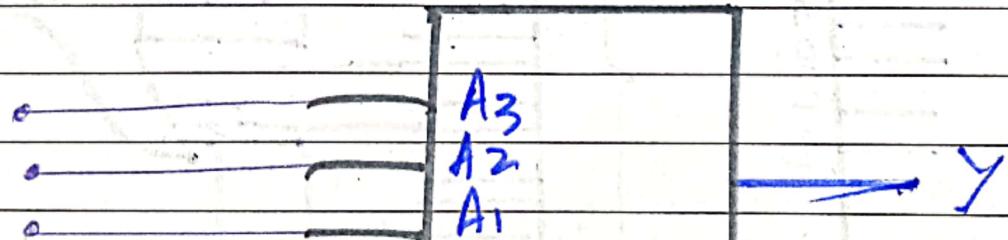

A_0

A_3
 A_2
 A_1


$\rightarrow Y$

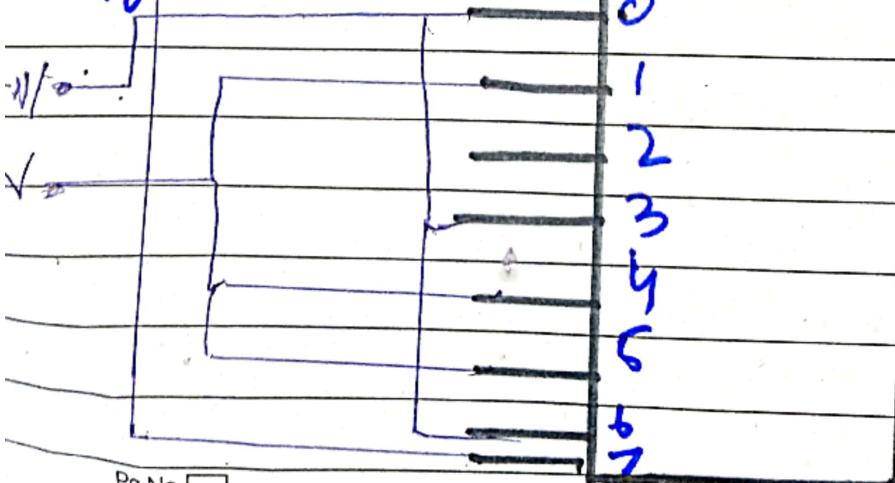


Question # 30

a) 3-to 8 Line Decoder:

A	B	Cin	Σ_1	Σ_2	out
0	0	0	0	0	0
0	0	1	1	0	0
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	0	1	0
1	1	0	0	1	0
1	1	1	1	1	1

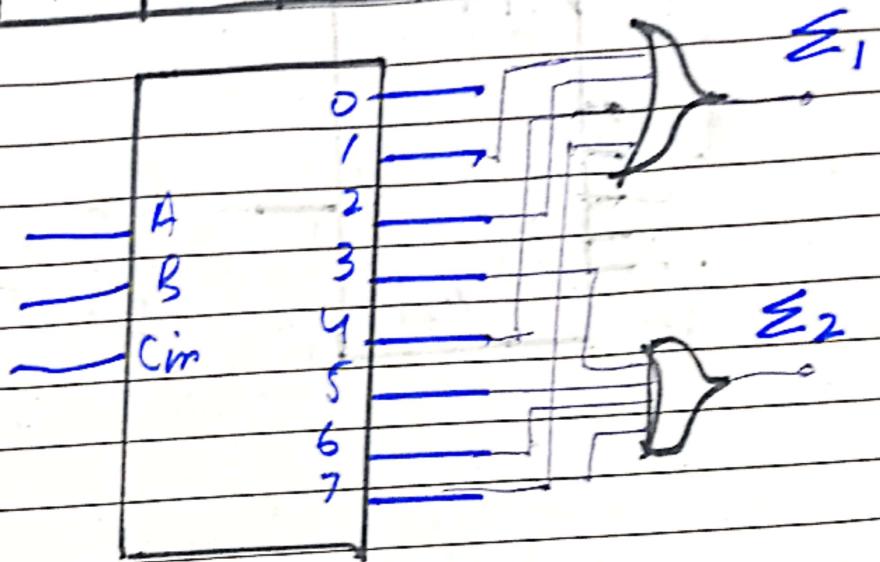

b) 4x1 Multiplexers:

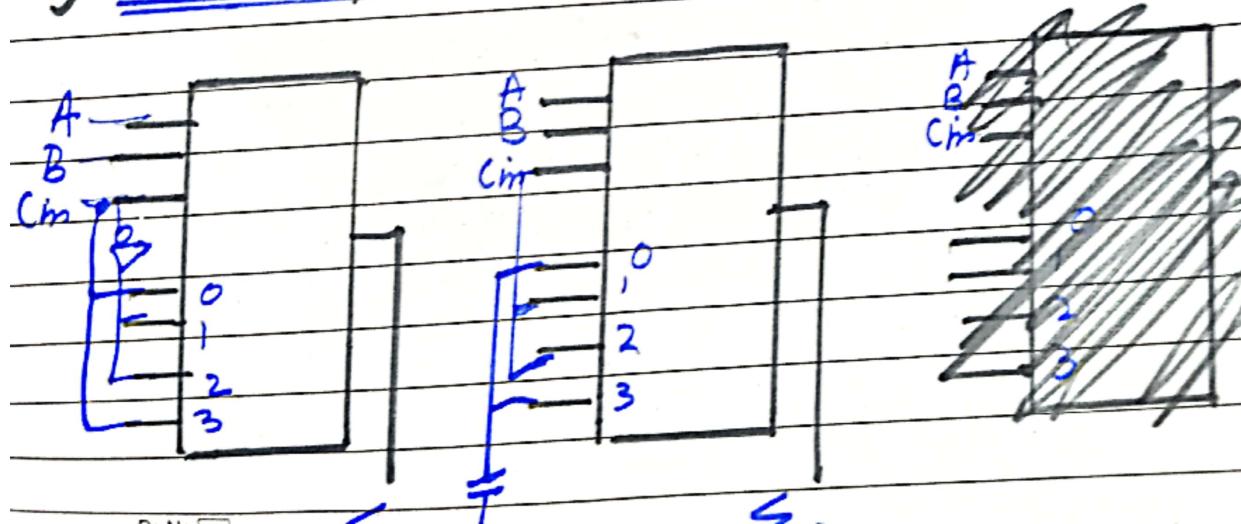

Date: _____

Question # 3)

