

Day / Date


DLD

20K-1077


Lab 11

Maleeha Khan

Lab Task #1

 


NAND

 


NOR gate

Using logic gates :-

 


NAND using logic gates :-

 


Lab Task #2


D latch

 

D latch using And and not:

 


D latch using OR and not:

 


Day / Date

TASK #3

NAND

 

NOR

 

Task #4

S	R	Q_n	Q	\bar{Q}	
0	0	0	Memory		
0	0	1	Memory		
0	1	0	0	1	Reset
0	1	1	Invalid		
1	0	0	1	0	Set
1	0	1	Invalid		
1	1	0	Invalid		
1	1	1	Invalid		