

Lab #3 Task

Name = Mukund Krishna
Roll-no = 20K-0409.

Task #1

3 input XOR and XNOR Gates,
Truth table and circuit diagram

3 - input XOR Gate

Truth table

A	B	$A \oplus B$	C	$(A \oplus B) \oplus C$
---	---	--------------	---	-------------------------

0	0	0	0	0
---	---	---	---	---

0	0	0	1	1
---	---	---	---	---

0	1	1	0	1
---	---	---	---	---

0	1	1	1	0
---	---	---	---	---


1	0	1	0	1
---	---	---	---	---

1	0	1	1	0
---	---	---	---	---

1	1	0	0	0
---	---	---	---	---

1	1	0	1	1
---	---	---	---	---


Symbol:

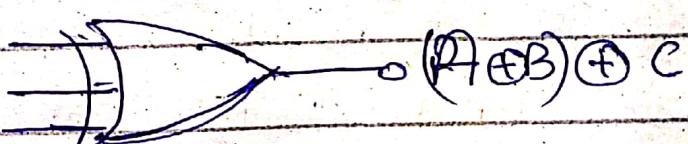

boolean expression


$$(A \oplus B) \oplus C = A\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B}C + ABC$$

Circuit diagram of 3-XOR gate.

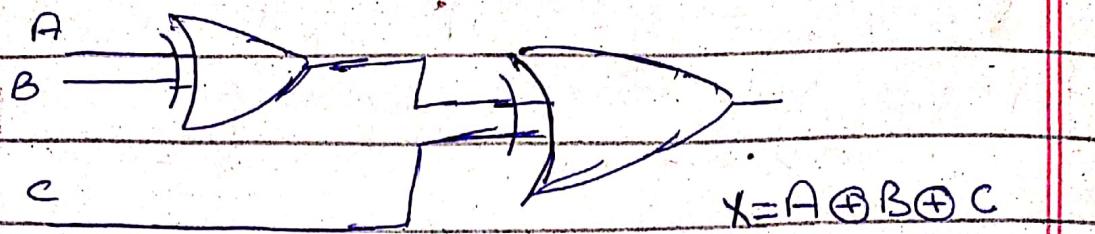

X-NOR Gate

Symbol:-

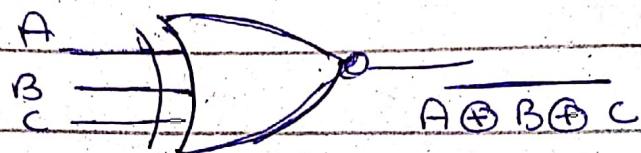

Boolean expression


$$X = \overline{A \oplus B \oplus C} \quad \text{OR}$$

$$X = \overline{\overline{ABC} + A\overline{BC} + A\overline{B}C + \overline{ABC}}$$

Truth table


A	C	B	$A \oplus B$	$A \oplus B \oplus C$	$\overline{A \oplus B \oplus C}$
0	0	0	0	0	1
0	1	0	0	1	0
0	0	1	1	1	0
0	1	1	1	0	1
1	0	0	1	1	0
1	1	0	0	0	1
1	0	1	1	0	1
1	1	1	1	1	0

circuit diagram

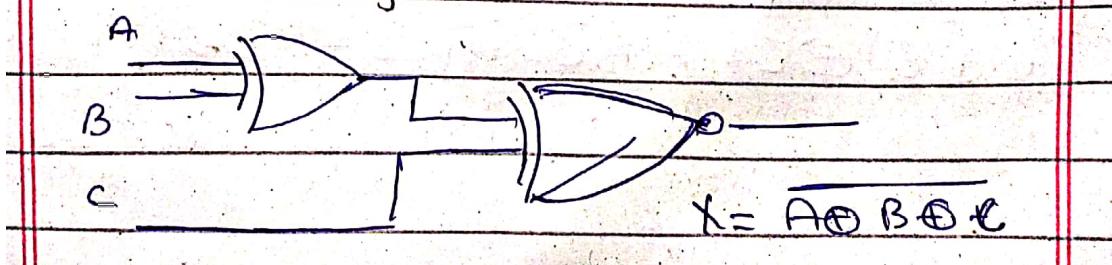

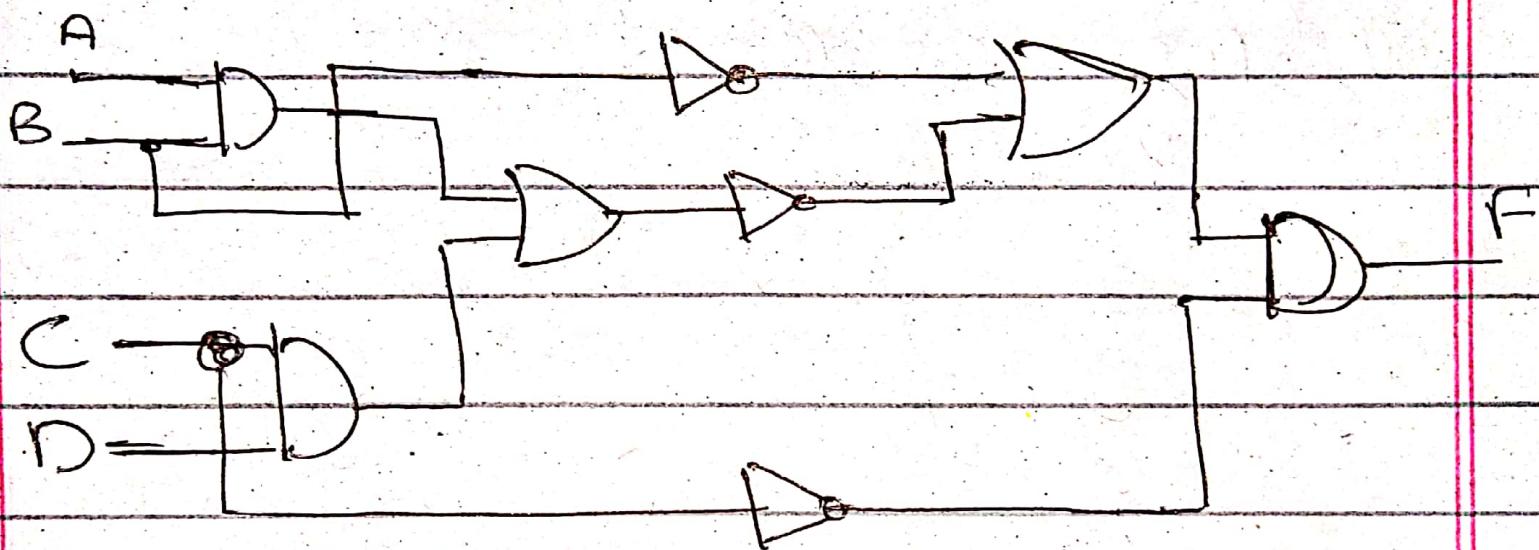Task #2.

Write Boolean expression of logic circuit.



1st step. $(A \cdot B), (C \cdot D)$

2nd " $(A \cdot B) + (C \cdot D)$.


3rd " $\bar{C}, \bar{B}, (A \cdot B) + (C \cdot D)$

4th " $(\overline{A \cdot B}) + (\overline{C \cdot D}) + \bar{B}$.

5th step. $((A \cdot B) + (C \cdot D) + \bar{B}) \cdot \bar{C}$

boolean expression

Task #3.

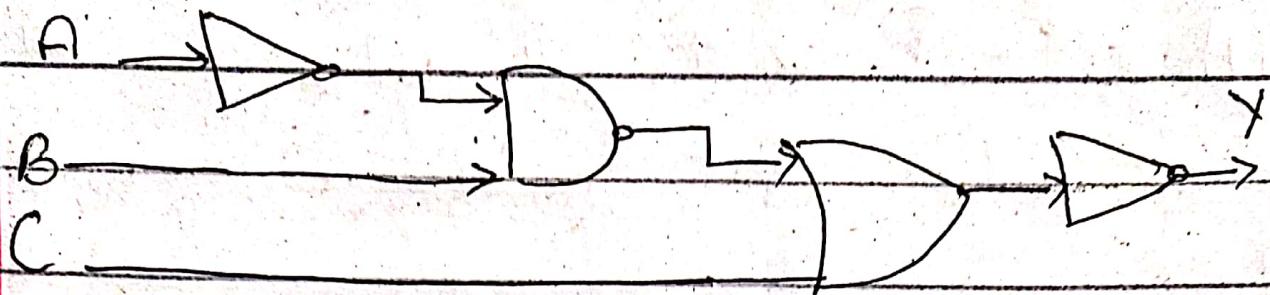


A	B	C	A'	$A \cdot B$	$(A \cdot B)'$	$(A \cdot B)' + C$	$((A \cdot B)' + C)'$
0	0	0	1	0	1	1	0
0	0	1	1	0	1	1	0
0	1	0	1	0	1	1	0
0	1	1	1	0	1	1	0
1	0	0	0	0	1	1	0
1	0	1	0	0	1	1	0
1	1	0	0	0	1	1	0
1	1	1	0	0	1	1	0

Boolean Expression:

$$((A' \cdot B)' + (A \cdot B)' + C)'$$

Task #4

1. $(A+B) \cdot (B+C)$

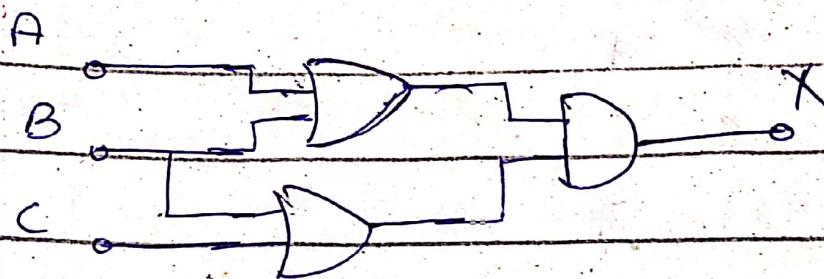


Truth table

A	B	C	$A+B$	$B+C$	$(A+B) \cdot (B+C)$
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	1	1	1
0	1	1	1	1	1
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	1	1	1
1	1	1	1	1	1

2. $(AB + C) \cdot D$.

circuit diagram.

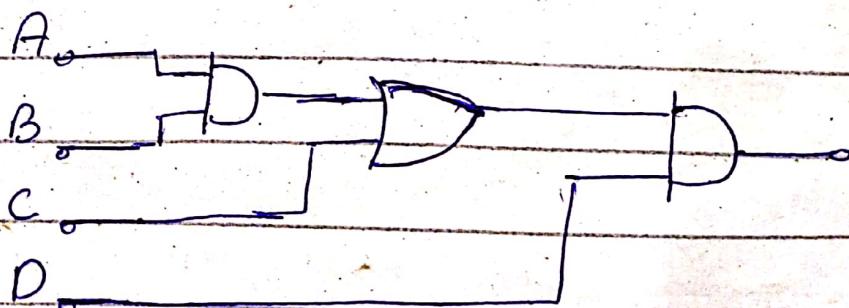


Truth Table

A	B	C	D	AB	$AB+C$	$(AB+C) \cdot D$
0	0	0	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	0	10	0
0	0	1	1	0	1	1
0	1	0	0	0	0	0
0	1	0	1	0	0	0
0	1	1	0	0	1	0
0	1	1	1	0	1	1
1	0	0	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	0	1	0
1	0	1	1	0	1	1
1	1	0	0	1	1	0
1	1	0	1	1	1	0
1	1	1	0	1	1	0
1	1	1	1	1	1	1

$$3. ((A+B'C) \cdot (A+BC))'$$

Circuit diagram

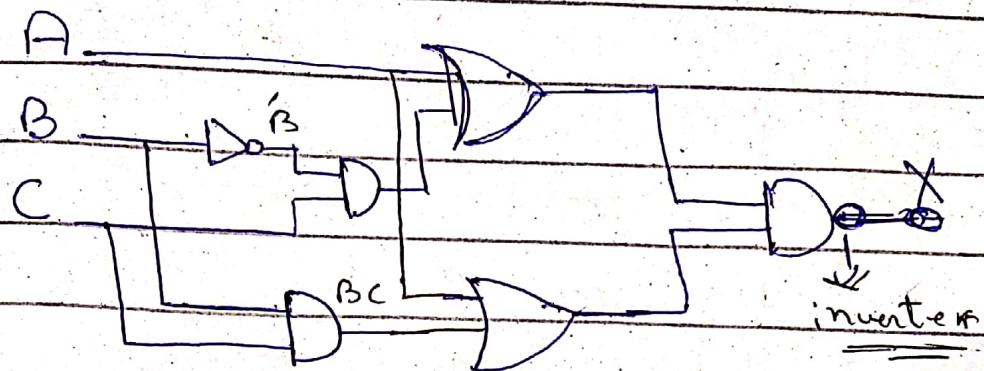

Truth table

B'	A	B	C	BC	$B'C$	$A+B'C$	$A+BC$	$(A+B'C) \cdot (A+BC)$
1	0	0	0	0	0	0	0	0
0	0	0	1	0	1	1	0	0
0	0	1	0	0	0	0	0	0
0	0	1	1	1	0	0	1	0
1	1	0	0	0	0	1	1	1
1	1	0	1	0	1	1	1	1
0	1	1	0	0	0	1	1	1
0	1	1	1	1	0	1	1	1

$$((A+B'C) \cdot (A+BC))'$$

1

1

1

0

0

0

0

$$4. A'B'C + AB'C' + ABC' + (ABC)'$$

circuit diagram

A	B	C	A'	B'	C'	\overline{BC}	$A'B'$
0	0	0	1	1	1	0	0
0	0	1	1	1	0	0	0
0	1	0	1	0	1	0	0
0	1	1	1	0	0	1	0
1	0	0	0	1	1	0	1
1	0	1	0	1	0	0	1
1	1	0	0	0	0	1	0
1	1	1	0	0	0	1	0

$$A \cdot B \quad AB'C \quad A'B'C \quad ABC' \quad ABc' \quad A \cdot B \cdot C$$

0	0	0	0	0	0
0	0	0	0	0	0
0	0	0	0	0	0
0	0	1	0	0	0
0	0	0	0	0	0
0	1	0	0	0	0
1	0	0	0	1	0
1	0	0	0	0	1


$$(A \cdot B \cdot C)' + (ABC)' + ABC' = A'B'C + AB'C$$

1	1	1
1	1	0
1	0	1
1	0	0
0	0	0

$$(A'B'C + AB'C) + (ABC' + (ABC)')$$

1
1
1
1
0


Circuit diagram.

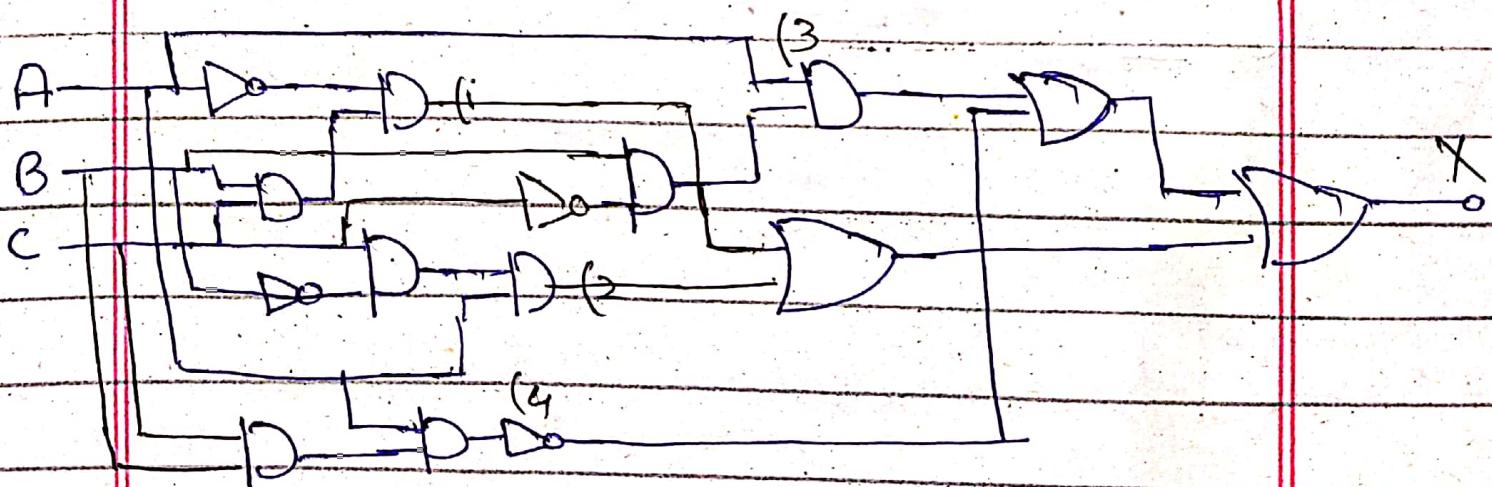

5. $(A' + B'C)'$

A	B	C	A'	B'	$B'C$	$A' + B'C$	$(A' + B'C)'$
0	0	0	1	1	0	1	0
0	0	1	1	1	1	1	0
0	1	0	1	0	0	1	0
0	1	1	1	0	0	1	0
1	0	0	0	1	0	0	1
1	0	1	0	1	1	0	1
1	1	0	0	0	0	0	1
1	1	1	0	0	0	0	1

circuit diagram.

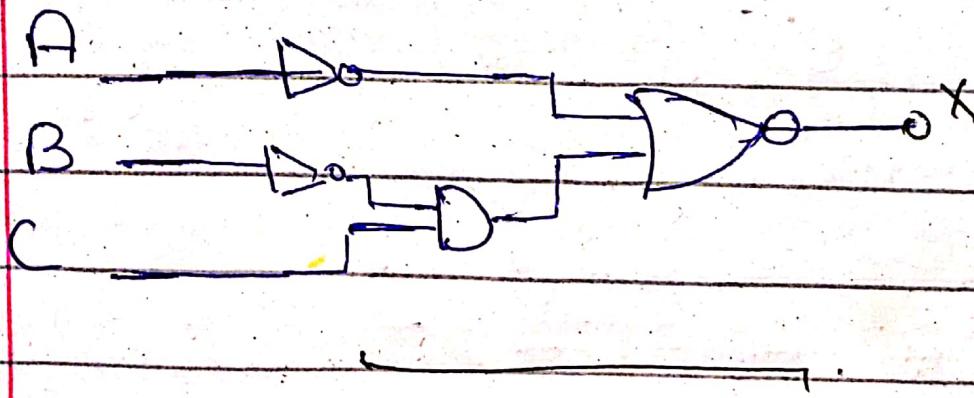

Task # 5.

c) Use Nand and NOR gates

ii) Given diagram of figure 9.

