

# Assignment #4.

Roll no: 20K-0409.

## Question 2

Solution.


Out of 16 there are 4 possible combination of inputs.

A	B	C	D	X
0	1	1	1	$\bar{A}BCD$
1	0	1	1	$A\bar{B}CD$
1	1	0	1	$AB\bar{C}D$
1	1	1	0	$ABC\bar{D}$

Expression :-

$$X = \bar{A}BCD + A\bar{B}CD + AB\bar{C}D + ABC\bar{D}.$$

## Circuit diagram.

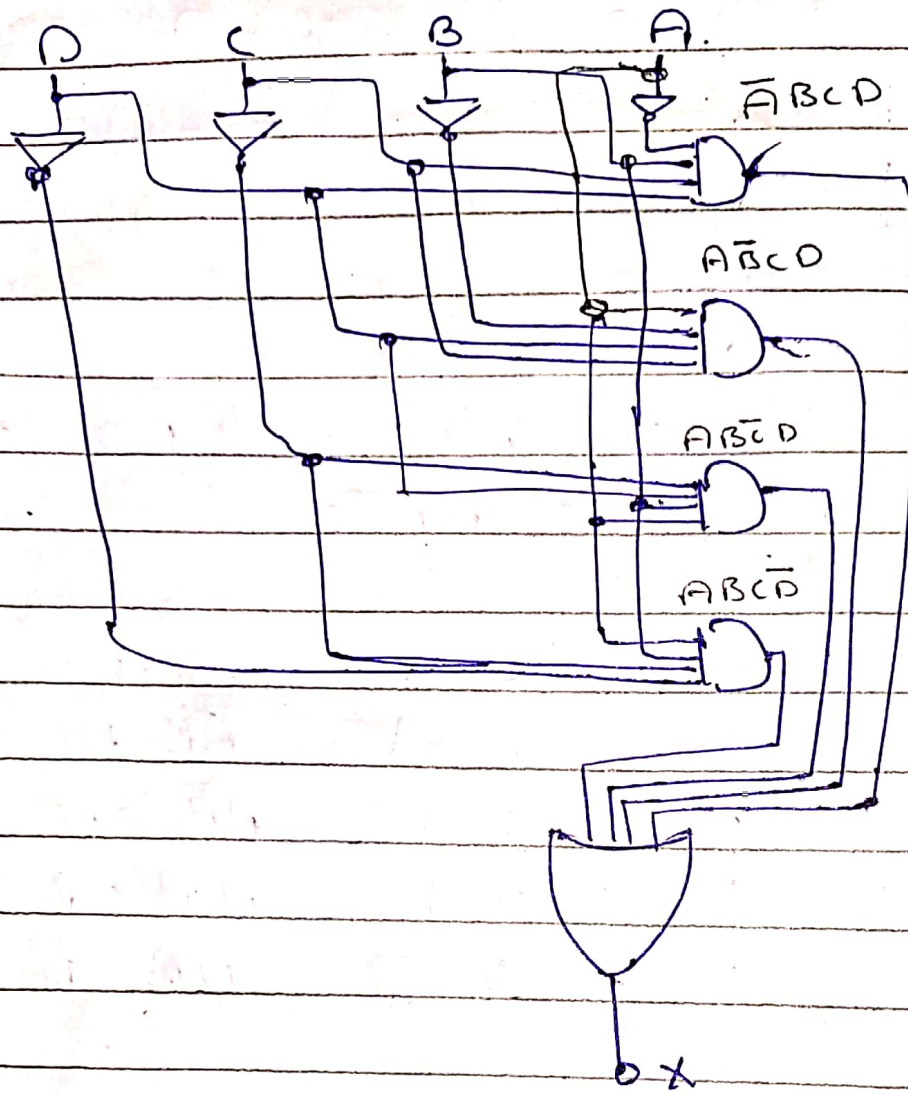

Question 3.

To convert from 6-bit binary code to gray code we can apply formula:-

$$B_5 = G_5 = B_5$$


$$G_4 = B_4 \oplus B_5$$

$$G_3 = B_3 \oplus B_4$$

$$G_2 = B_2 \oplus B_3 \quad G_1 = B_1 \oplus B_2$$

$$G_0 = B_0 \oplus B_1$$

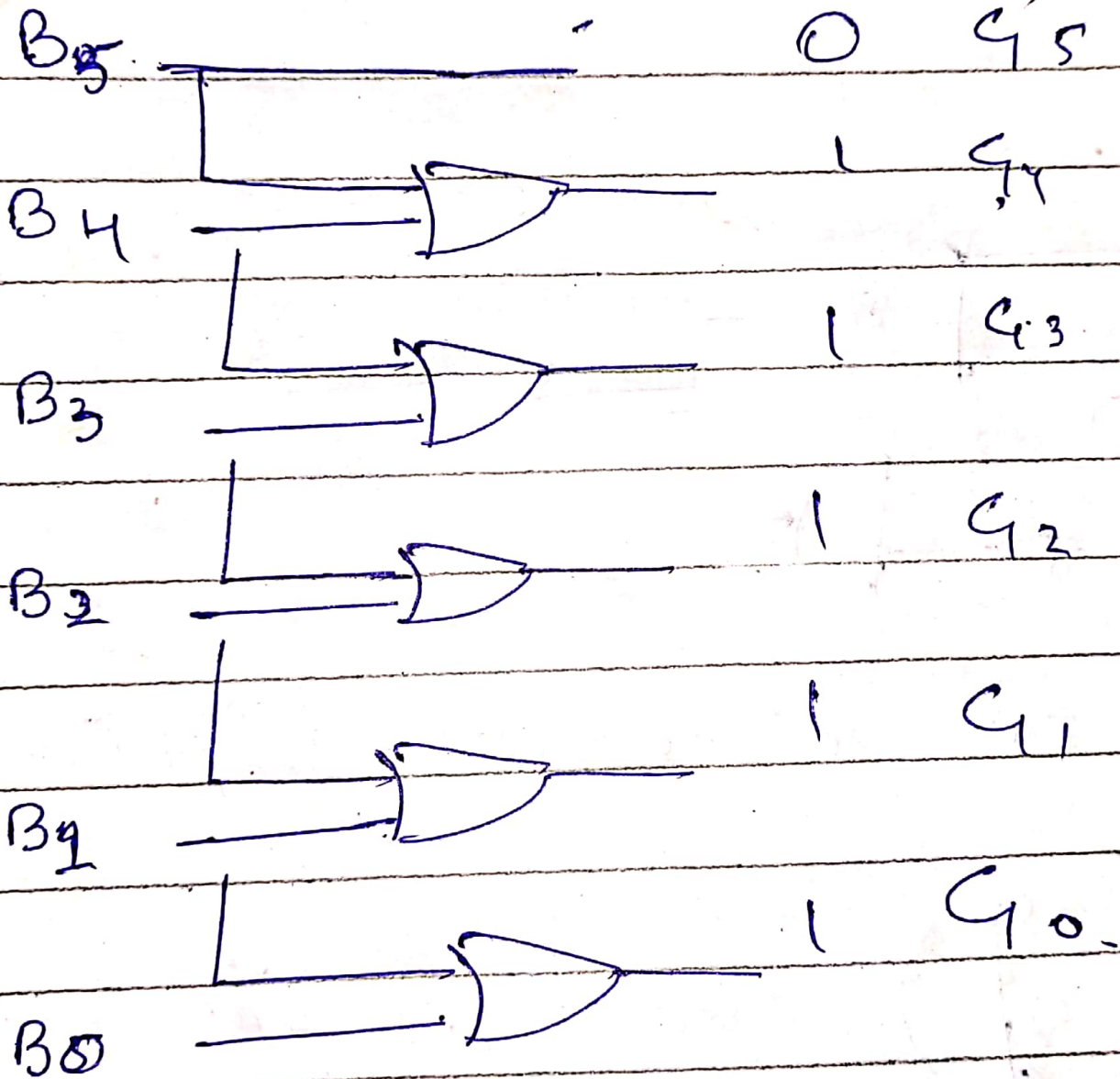For example  $\overset{B_5}{0} \overset{B_4}{1} \overset{B_3}{0} \overset{B_2}{1} \overset{B_1}{0} \overset{B_0}{1} \rightarrow C(D)$   
 $B_5 B_4 B_3 B_2 B_1 B_0$




$$0 \ 1 \ 1 \ 1 \ 1 \ 1 = C(D)$$






## Question no 1

Modifying circuit diagram  
from.

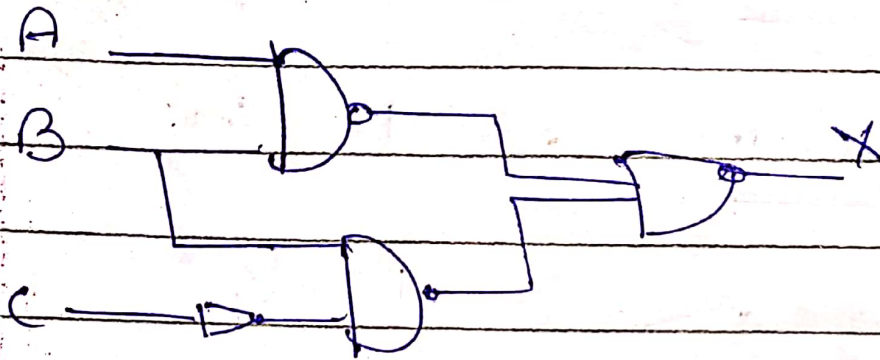

For active-low output.

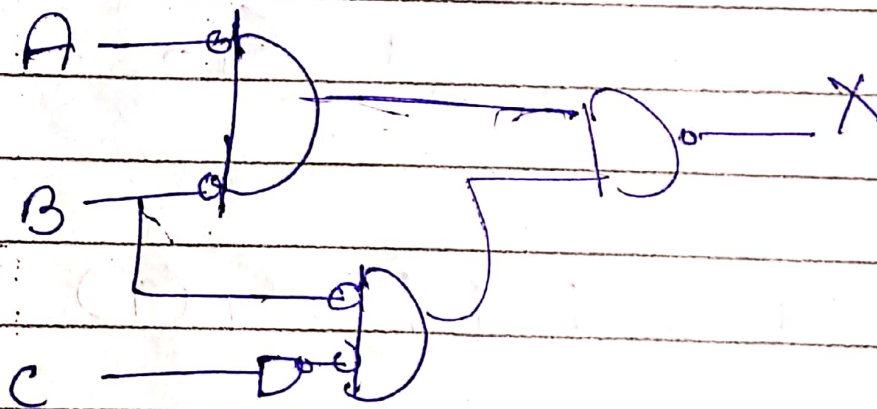

Explanation: output would  
be low when A and B  
are low OR when B  
and C is high.

